

Fashioning Circuits Oct 31

serial vs. parallel LEDs tri-color LEDs fade and forloopiteration

Serial vs. Parallel Wiring

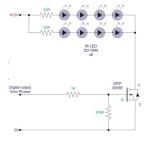

Serial vs. Parallel Wiring

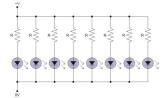


Tri-color LED



- Three colors Red, Blue, Green
 - "color changing" = 1 LED with 3 petals.

Tri Color LEDs

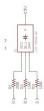

Tri-Color LED







Adafruit Smart NeoPixel

Exercises

- Connect RGB LED to a button or switch
- Play with Fade with RGB